

## APPLICATION NOTES

# PCB Logic Clock Design for Low DPPM

Application specific integrated circuits (ASICs), with an internal oscillator cell, benefit from the proper selection of five external capacitors, resistors and crystal load to increase frequency stability, reduce cost, and reduce defective parts per million (DPPM).

### Barkhausen Rules

For oscillation to occur, two Barkhausen rules must be applied:

- The summation of the phase shifts around a closed loop must be  $n \times 360^\circ$  where  $n$  is an integer
- Summation of the gains around a closed loop must be  $\geq 1$

### Crystal Equivalent Circuit

Figure 1 is the equivalent circuit for a crystal plus external load.

### Oscillator Schematic

Most ASIC use the Pierce oscillator configuration – see Figure 2.

### Pi Capacitors

Pi capacitive reactance values should be in the low hundreds of ohms approximately equal to the output impedance of the ASIC cell. Oscillator cells designed for lower frequency AT-cut crystals have  $\sim 300\text{-}500 \Omega$  Thevenin output resistance ( $R_{out}$ ).


Higher frequency fundamentals are  $\sim 100\text{-}300 \Omega$ .

- Pi caps are changed as a function of crystal load and VDD
- Pi caps are usually the same value or C1 may be slightly smaller than C2 – see Table 1


**TABLE 1**

CRYSTAL LOAD	+3.3 VDC		+5 VDC	
	C1	C2	C1	C2
6	5	6		
7	8	8		
8	10	10	5	5
10	12	15	6	8
11	15	18	8	10
12	18	22	10	12
14	22	22	15	15
16	22	27	18	22
18	27	33	22	27
20	33	39	27	27
22	39	39	33	33
30	56	56	47	47
32	56	68	47	56

**FIGURE 1**

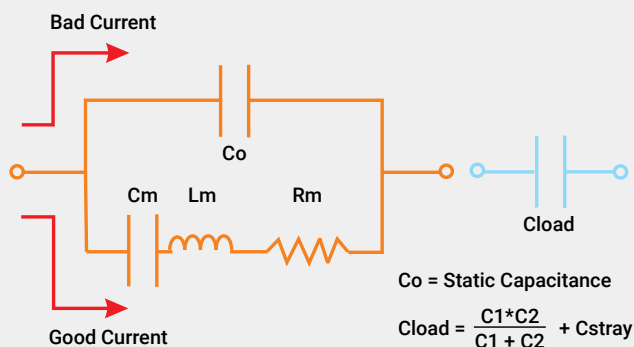

**FIGURE 2**

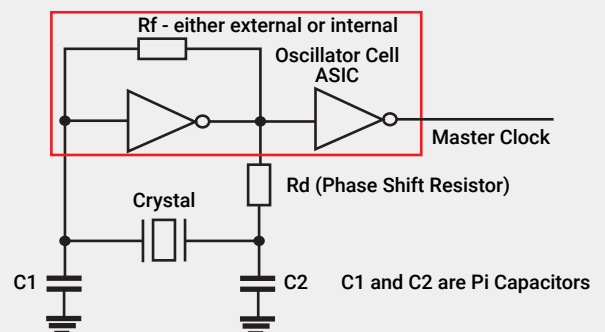


### Rd Selection

Rd, sometimes called a phase shift resistor, is between IC output and crystal. It has four specific functions:

- Reduce crystal power
- Reduce C2 output loading
- Shift phase
- Increase frequency stability

If Rd equals Xc2, a Bode plot would show there is a fast rate-of-change of phase at the 360° oscillation requirement. Fast rate-of-change of phase is critical for good frequency stability – see Figure 3.

**FIGURE 3**

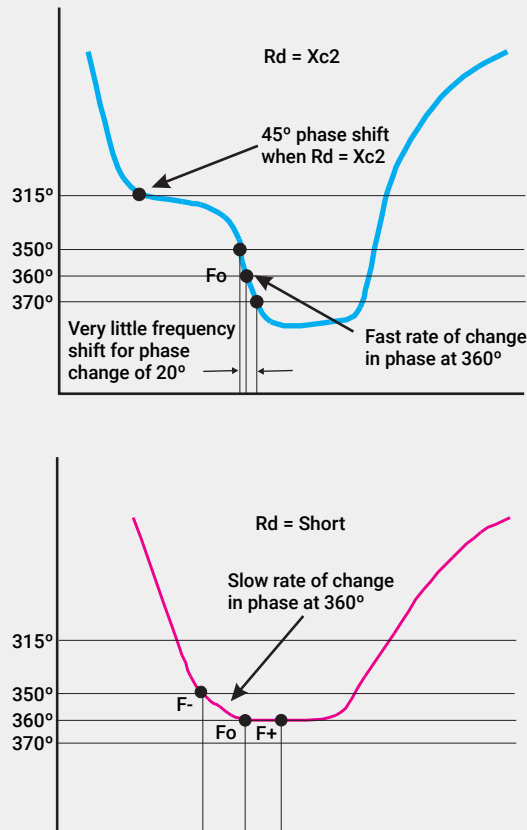

Rout and Rd are in series. The series combination is in parallel with C2. Select Rd = Rout = Xc2 unless cell has insufficient drive capability. First select C2, then select Rd.

Rout in series with Rd are shunting C2 (Rout + Rd) // Xc2). With Rd=Rout=Xc2, we have a loaded Q of only 2. Design for Q of 2, but you may accept a Q of 1.

### Rf Selection

Most ASICs have an internal Rf resistor. Choose an Rf value between 100k and 500k Ω if one is not available.

### Crystal Load

With a good oscillator PCB layout and VDD = +5 VDC, Cstray is ~6 to 7 pf. With VDD = +3.3 VDC or lower, Cstray is ~3 pf.

$$\text{Cload} = \frac{C1 \cdot C2}{C1 + C2} + \text{Cstray}$$

### Crystal Load vs Frequency

Crystal load is a function of frequency. Suggested values are in Table 2.

**TABLE 2**

LOAD	FREQUENCY RANGE
20 PF	---> 5 MHZ
18 PF	5 TO 10 MHZ
16 PF	10 TO 15 MHZ
14 PF	15 TO 20 MHZ
12 PF	20 TO 30 MHZ
10 PF	30 TO 40 MHZ
8 PF	40+ MHZ

### C1, C2 Selection

Figure 1 has C1 and C2

calculations for specified loads.

Stray capacitance has many variables; however, Table 1 can be used to get most crystals close to the proper frequency.

### Circuit Waveshape Verification

Check circuit waveshapes with a non-loading FET probe (or equivalent). With Rd=Rout=Xc2, the top of C2 should be a poor man's sinewave. Peak to peak amplitude should be ~70% of VDD.

If Rd is omitted (sometimes done at higher frequencies or with low output drive), layout should still include Rd as a short. If Rd is a short, the top of C2 should be a square

wave with rounded corners. Sharp rise and fall times are indications of excessively high drive or insufficient C2. If C2 is too small, a low resistance crystal may have high ESR.

$$ESR = Rm * \left( 1 + \frac{Co}{Cload} \right)^2$$

Less than a full amplitude square wave is an indication that Rd may be too large or C2 may be too large and is passing a signal to ground.

### Starting Voltage Checks

Continuously monitor the wave shape at the IC output for any abnormalities during all starting tests. This may be difficult on a PCB unless the PCB regulated supply is overridden.

Low voltage starting checks should be made by slowly increasing VDD from 0 volts. Perform this test first to detect and prevent the effects of a sleepy crystal. The oscillator should be started at half the nominal VDD; if not, loading on the IC may be too large or the IC may have insufficient gain. Continue testing up to nominal VDD plus 1.5 VDC.

High voltage starting checks are made by applying numerous VDD step functions beginning with VDD plus 1.5 VDC and slowly decreasing to low voltage starting point. Intermittent starting problems may be an indication that Co or Cstray are too large.

Medium voltage starting checks are made by switching the power supply switch on and off. Perform this test from half VDD to VDD plus 1.5 V.

### Negative Resistance Testing

Negative resistance is similar to circuit gain. Test the circuit by installing a resistive potentiometer in series

with an average crystal. Do not perform this test on a known bad crystal. Negative resistance is the value of the potentiometer plus the crystal's series resistance.

$$-r = Rpot + Rs$$

### Crystal Power

While the crystal is disconnected, attach a current probe and measure crystal current. Do not exceed maximum rated power of the crystal unit.

$$\text{Crystal Power} = Irms^2 * Rm$$

### Adjusting -r

Where gm is the transconductance of the inverter:

$$-r = gm * \left( \frac{1}{\omega C1} + \frac{1}{\omega C2} \right) \quad \omega = 2 \pi \text{ frequency}$$

By making C1 and C2 smaller, we can raise the negative resistance. Caps too small will cause high ESR and reduced phase shifting.

### Circuit Margin

Circuit margin is defined as the absolute value of negative resistance |-r| divided by the average value of ESR.

$$CM = \frac{|-r|}{ESR_{avg}}$$

For low DPPM, circuit margins should be at least 10. Some approximate values taken from experimental data can be found in *Table 3*.

**TABLE 3**

CKT MARGIN	EXPECTEDDPPM
1.5	Runs poor w/ best xtals
2	Serious operating pblms
3	Intermittent starting
5	- 1,000 dppm
10	- 100 dppm
15	- 25 dppm
20	- 15 dppm
25	Single digit dppm

### Temperature Testing

Quick temperature testing can be performed using a few seconds of freeze mist (or a can of duster spray held upside down) and a hair dryer. Test only when circuit is returning to room temperature.

### Summary

Oscillator designers and crystal suppliers working together can assemble circuits having single digit DPPM failure rates. This starts with the oscillator being designed on sound basics and working with a crystal supplier that designs, manufactures and controls production. On initial designs, it is suggested that the schematic or the PCB should be sent to the crystal supplier for circuit board matching.



World-Class Manufacturer of High-Quality Frequency Control Solutions for the Global Electronics Industry